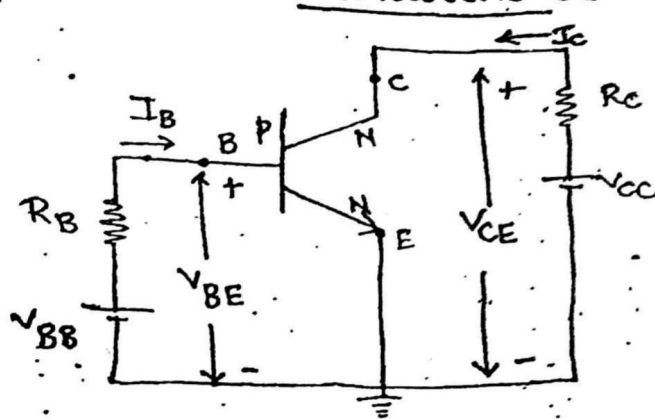


Common Emitter characteristics:-



$$V_{CC} \gg V_{BB}$$

Inputs (V_{BE}, I_B)

o/p (V_{CE}, I_C)

For a BJT Transistor

Dependents (V_{BE}, I_C)

Independents (V_{CE}, I_B)

i/p char.

$$V_{BE} = f[I_B, V_{CE}]$$

$$I_C = f[I_B, V_{CE}]$$


o/p char.

Input characteristics:-


V_{BE} vs I_B when $V_{CE} = \text{const}$

- (i) C & E \rightarrow o.c
- (ii) C & E \rightarrow s.c i.e $V_{CE} = 0V$
- (iii) $V_{CE} \neq 0V$

Case (i): when 'C & E' \rightarrow o.c

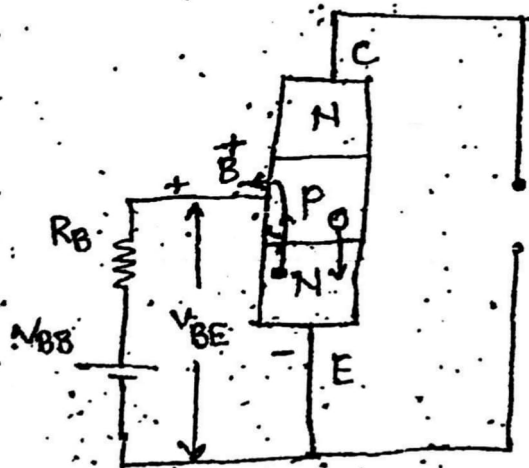


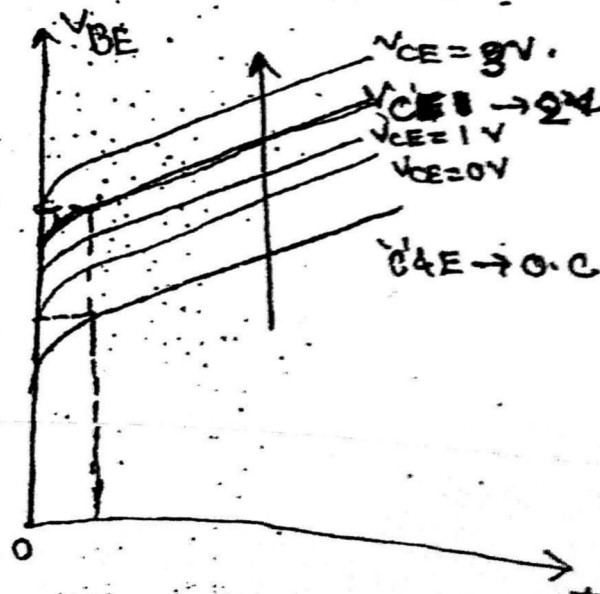The char. of the transistor in this case is similar to the char. of a F-B PN junction diode with axes interchanged.



Case (i) when $V_{CE} = 0V$

$$V_{CE} = 0V$$

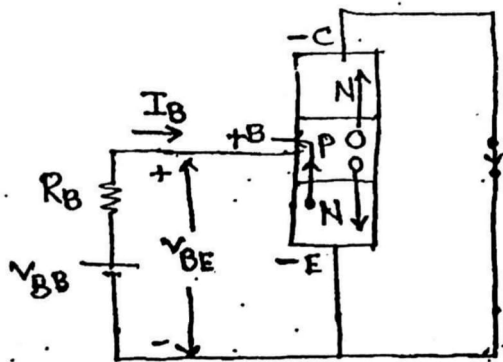


* All the maj. carriers of E' collected by B' . There is no change in current due to \bar{e}' b/w B' & E' in case (i) & case (ii)

* The no. of holes collected by the E' from the Base \downarrow
 \therefore The hole current b/w B' & $E' = \downarrow$

* To maintain I_B as const. increases the V_{BE} value.
 i.e. to get a particular value of I_B the req. value of V_{BE} is more in this case compared to case (i).

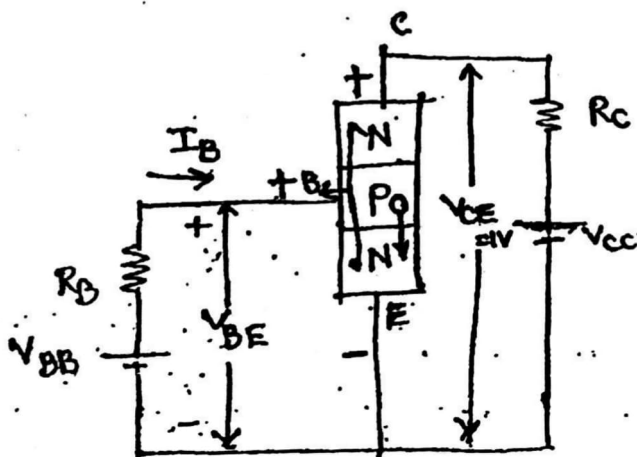Case (iii) when $V_{CE} \neq 0$ Let $V_{CE} = 1V$.



$$V_{BE} = V_{\gamma}$$

$$V_B - V_E = V_{\gamma}$$

$$V_B = V_{\gamma} + V_E$$

$$V_C = 1 + V_E$$

$$V_C > V_B$$

* The no. of \bar{e}' s collected by B' from E' \downarrow

The \bar{e} current b/w B' & E' \downarrow

The no. of holes collected by E' from B \uparrow .

The hole current b/w B' & E' \uparrow

\therefore The resultant current B' & $E' \downarrow$, $I_B \downarrow$

To maintain I_B as constant $\uparrow V_{BE}$ i.e. to get a


Particular value of I_B the required value of V_{BE} is more in this case compared to case (i).

output characteristics:-

$$I_C \text{ vs } V_{CE} \text{ when } I_B = \text{const} \begin{cases} I_B = 0 \\ I_B \neq 0 \end{cases}$$

Case (i):- when $I_B = 0$

→ B & E terminals are O.C

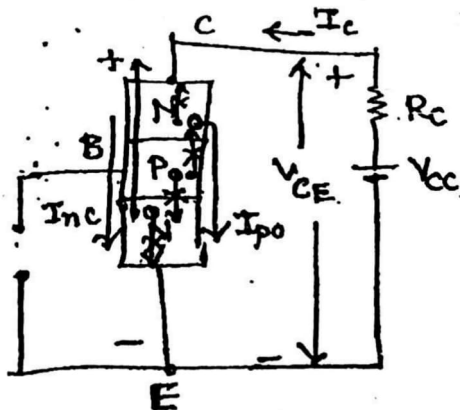


$$I_C = I_{nC} + I_{pO}$$

As $V_{CE} \uparrow$ $I_C \uparrow$

case (ii):- when $I_B \neq 0$

Let $I_B = 5 \mu A$.

' J_E ' must be $F \cdot B$

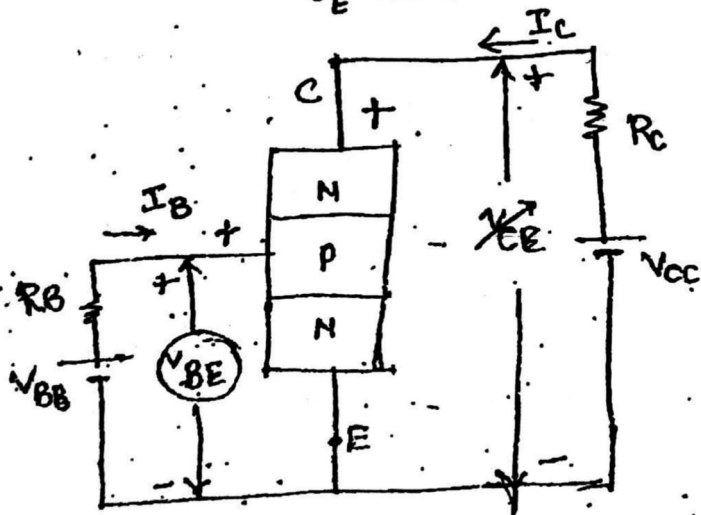

$$V_{CE} = 0$$

$$V_C = V_E$$

$$V_B = V_{BE} + V_E$$


As $V_{CE} \uparrow$

(i) when $V_{CE} < V_{BE} \Rightarrow I_C \rightarrow F \cdot B$

→ saturation Region.

(ii) when $V_{CE} > V_{BE} \Rightarrow I_C \rightarrow R \cdot B$

→ Active Region.

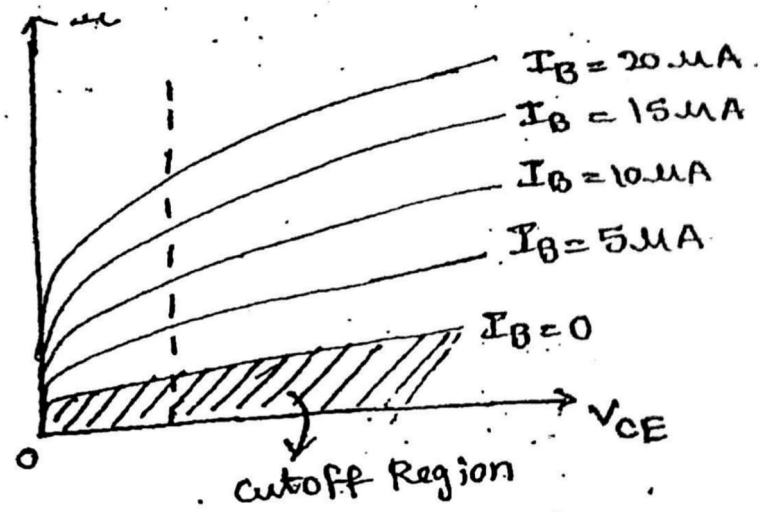

* The common collector characteristics are similar to common emitter characteristics. In i/p characteristics V_{BE} replaced by V_{CB} . In o/p characteristics I_C replaced by I_E .

* The phase shift b/w i/p & o/p for

(i) CB $\rightarrow 0^\circ$

(ii) CE $\rightarrow 180^\circ$

(iii) CC $\rightarrow 0^\circ$

* CB $\left\{ \begin{array}{l} \text{i/p} \rightarrow I_E \\ \text{o/p} \rightarrow I_C \end{array} \right\} \Rightarrow +I_C = +I_E - I_B$
 $\curvearrowright 0^\circ$

* CE $\left\{ \begin{array}{l} \text{i/p} \rightarrow I_B \\ \text{o/p} \rightarrow I_C \end{array} \right\} \Rightarrow +I_C = +I_E - I_B$
 $\curvearrowright 180^\circ$

* CC $\left\{ \begin{array}{l} \text{i/p} \rightarrow I_B \\ \text{o/p} \rightarrow I_E \end{array} \right\} \Rightarrow +I_E = +I_C + I_B$
 $\curvearrowright 0^\circ$