 


## Unit-5 Verilog Program -Combinational and Sequential

03 September 2022 13:26

### Verilog Program



Understand the meaning of following code.

```
module test_wave();
reg A, B;


initial
begin
    //Start of initial block
    // both a and b are initialised at 0th time unit
    A = 1'b0;
    B = 1'b1;
    #5    A = 1'b1;        //A changes at 5th time units
    #8    B = 1'b0;        //B changes at 5 + 8 = 13th time unit
    #10{B, A} = 2'b10;    //again both B & A changes at 5 + 8 + 3 = 23rd time
                           //unit. See the use of concatenation {}.
end
//End of initial block
endmodule
```


Use of 'for' loop to generate a test pattern.

```
module for_loop();
reg [3:0] din;

integer i;

 initial
begin
    for (i=0; i<= 15; i = i+1)
    begin
        //multiple statements must be
        //encapsulated within begin...end
        din = i;
        #10;
        //increment 'i' after the delay of 10
        //time units
    end
    //end of the for loop
end
endmodule
```



 

## Module Instantiation

There are two types of instantiation constructs in Verilog

### Positional Instantiation:


`child_module_name [optional_instance_name] (comma_seperated_list_of_the_signals);`

Child module name is the name of the black box to be instantiated.

**Named Instantiation:** Both child- and parent- module port names are used in this method of instantiation. Therefore, the order of ports is immaterial.

`child_module_name [optional_instance_name] (.child_port_1(parent_port_1),  
.child_port_2 (parent_port_2), ...);`

 **Q.1. Write a structural Verilog to implement gets Given in Figure Also write Test bench to test of the behavior of the gates.**



```
module basic_gates (A,B,C,in, N_O, A_O, O, 01, 02, 03); /* include all
input and output terminals */
```

```
input A, B, C, in;
```

```
output N_O, A_O,O,01,02,03;
```

```
nor (N_O, A,B,C); //first terminal is always output than write inputs
```

```
and (A_O, A, B,C);
```

```
not (O,in) ;
```

```
buf (01, 02, 03,in);
```


```
Endmodule
```

```
module basic_gates_tb();
reg A, B, C, in;
wire N_O, A_O, O1, O2, O3;
basic_gates u (A, B, C, in, N_O, A_O, O1, O2, O3); //DUT is instantiated using
positional instantiation


initial //Applying stimuli to 3 input gates
begin //Use of concatenation {} operator.
{A, B, C} = 3'b000;
#10 {A, B, C} = 3'b001;
#10 {A, B, C} = 3'b010;
#10 {A, B, C} = 3'b011;
#10 {A, B, C} = 3'b100;
#10 {A, B, C} = 3'b101;
#10 {A, B, C} = 3'b110;
#10 {A, B, C} = 3'b111;
end

initial //Applying stimuli to 1 input gates
begin
in = 1'b0;
#20 in = 1'b1;
#20 in = 1'b0;
#20 in = 1'b1;
end
endmodule
```

## Simulation webform

 

 **Q.2. Write a structural Verilog code to implement half adder circuit shown in Fig. write the test bench to verify the functionality of design.**



```

module half_adder (A, B, S, C);
input A, B;
output S, C;

xor (S, A, B);
and (C, A, B);

endmodule

module half_adder_tb();

reg a, b;
wire s, c;


half_adder u (.A(a), .B(b), .S(s), .C(c)); //DUT is instantiated using named
                                             instantiation

    initial
    begin
        {a,b} = 2'd0; //use of decimal numbers
        #10 {a,b} = 2'd1;
        #10 {a,b} = 2'd2;
        #10 {a,b} = 2'd3;
    end


endmodule

```

Waveform

 

 Q.3. Write a structural Verilog code to implement half subtractor circuit shown in figure. Also write test bench.



```

module half_subtractor (A, B, D, C);
input A, B;
output D, C;

```

```

module half_subtractor_tb();

reg a, b;
wire d, c;

half_subtractor u (.A(a), .B(b), .D(d), .C(c)); //DUT is instantiated using
                                             named instantiation

    initial
    begin
        {a,b} = 2'd0; //use of decimal numbers
    end

```

```

module half_subtractor (A, B, D, C);
input A, B;
output D, C;

xor (D, A, B);
not (A_bar, A);
and (C, A_bar, B);

endmodule

```

```

half_subtractor u (.A(a), .B(b), .D(d), .C(c)); //named instantiation


initial
begin
    (a,b) = 2'd0; //use of decimal numbers

#10 (a,b) = 2'd1;
#10 (a,b) = 2'd2;
#10 (a,b) = 2'd3;
end

endmodule

```

 Q.4. Write a structural Verilog code to implement 4:1 multiplexer circuit. Also write test bench code.



```

module mux_4_1 (S0, S1, I0, I1, I2, I3, Y);
input S0, S1, I0, I1, I2, I3;
output Y;

not (s1_bar, S1);
not (s0_bar, S0);
nand (y0, I0, s1_bar, s0_bar);
nand (y1, I1, s1_bar, S0);
nand (y2, I2, S1, s0_bar);
nand (y3, I3, S1, S0);
nand (Y, y0, y1, y2, y3);

endmodule

```

```

module mux_4_1_tb ();
reg S0, S1, I0, I1, I2, I3;
wire Y;
mux_4_1 u (S0, S1, I0, I1, I2, I3, Y);

initial
begin
    {S1, S0} = 2'd0;
    {I3, I2, I1, I0} = 4'h0;


#15 I0 = ~I0;
#15 I0 = ~I0;

#20 {S1, S0} = 2'd1;
#15 I1 = ~I1;
#15 I1 = ~I1;

#20 {S1, S0} = 2'd2;
#15 I2 = ~I2;
#15 I2 = ~I2;

#20 {S1, S0} = 2'd3;
#15 I3 = ~I3;
#15 I3 = ~I3;
end
endmodule

```

 

02 September 2022  
21:48

## Behavioral (Algorithmic) Coding Examples

Write behavioral Verilog code to implement positive edge triggered D flip-flop.

```

module d_FF (input clk, d, output reg q, output q_bar);

    assign q_bar = !q;

    always @(posedge clk)
        q <= d;

endmodule

```

Test bench

```


module d_FF_tb ();
reg clk, d;
wire q, q_bar;

d_FF u (clk, d, q, q_bar);

always
#10 clk = ! clk;

initial
begin
    clk = 1'b0;
    d = 1'b0;
#35 d = !d;
#28 d = !d;
#12 d = !d;
#20 d = !d;
end
endmodule

```

 

write behavioral code to implement negative edge triggered T Flip flop with synchronous active low clear input.

```

module T_ff(input clk, T, Clear, output reg q);
always @ (negedge clk)
begin
    if (~Clear)
        q = 1'b0;
    else if (T)
        q = ~q;
end
endmodule

module T_ff_tb();
reg clk, T, Clear;
wire q;

T_ff u (clk, T, Clear, q);

always
#10 clk = ! clk;

initial
begin
    clk = 1'b0;
    Clear = 1'b1;
    T = 1'b1;
#15 Clear = 1'b0;
#33 Clear = 1'b1;
#30 T = !T;
#27 T = !T;
end
endmodule

```

