

Experiment : 4

PARALLEL ADDER

Aim: To design and set up the 4 bit binary adder and Subtractor.

Learning objective:


- To learn about IC 7483 and its internal structure.
- To realize a Subtractor using adder IC 7483.

Components required: IC 7483, IC 7486 trainer kit, patch cords.

Theory:

The Full adder can add single-digit binary numbers and carries. The largest sum that can be obtained using a full adder is 11_2 . Parallel adders can add multiple-digit numbers. If full adders are placed in parallel, we can add two- or four-digit numbers or any other size desired. Figure below uses standard symbols to show a parallel adder capable of adding two; two-digit binary numbers. The addend would be on A inputs, and the augend on the B inputs. For this explanation

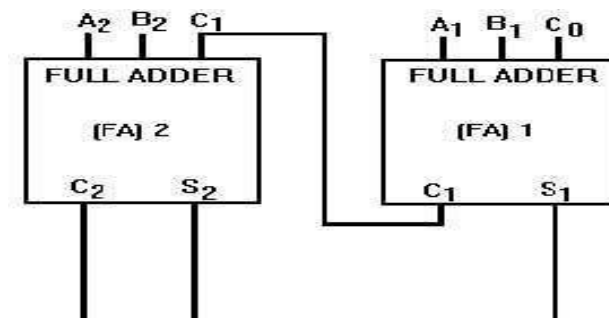we will assume there is no input to C_0 (carry from a previous circuit)



To add 10_2 (addend) and 01_2 (augend), the addend inputs will be 1 on A₂ and 0 on A₁. The augend inputs will be 0 on B₂ and 1 on B₁. Working from right to left, as we do in normal addition, let's calculate the outputs of each full adder. With A₁ at 0 and B₁ at 1, the output of adder1 will be a sum (S₁) of 1 with no carry (C₁). Since A₂ is 1 and B₂ is 0, we have a sum (S₂) of 1 with no carry (C₂) from adder 1. To determine the sum, read the outputs (C₂, S₂, and S₁) from left to right. In this case, C₂ = 0, S₂ = 1, and S₁ = 1. The sum, then, of 10_2 and 01_2 is 011_2 .

Circuit implementation:


4 Bit Binary Adder:

An Example: $7+2=9$ (1001)

7 is realized at A₃ A₂ A₁ A₀ = 0111

2 is realized at B₃ B₂ B₁ B₀ = 0010

Sum = 1001

 

Truth table:

Inputs A				Inputs B				Sum			
A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	S ₃	S ₂	S ₁	S ₀
0	1	1	1	0	0	1	0	1	0	0	1

Procedure:

- Check the components for their working.
- Insert the appropriate IC into the IC base.
- Rig up the circuit as shown in the logic circuit diagram.
- Apply various input data to the logic circuit via the input logic switches.
- Note down the corresponding output and verify the truth table.

Result: Hence parallel adder designed and implemented successfully.

